



UNITED STATES
AIR FORCE
ACADEMY

ECE 383 - Embedded
Computer Systems II
Lecture 4 - Sequential
Element

versus

Combinational?



Using Unsigned and Decimal Numbers

- Convert Decimal number to Unsigned Vector (7 downto 0)

`to_unsigned(17, 8)`

- First argument is the decimal number
- Second argument is the number of bits

17
8




- Conditional with unsigned number

```
LED_Trigger <= '1' when (Binary_Input = to_unsigned(17, 8) ) else  
    '0';
```



 1. Sequential Elements
2. **Mod 10 Counter Example**
 - Truth Table
 - Timing Diagram
 - Circuit Diagram
 - VHDL
3. **General VHDL Rules**
4. **Adding Signals to Vivado**



Homework #4




UNITED STATES
AIR FORCE
ACADEMY

Sequential Elements

Sequential Elements

- Goals:
 - basic sequential process and sensitivity list
 - register, counter in VHDL
 - Combination of sequential and combinational logic (counters)
 - Translate between schematic, truth table, and VHDL code

flip flop
vs
latch?

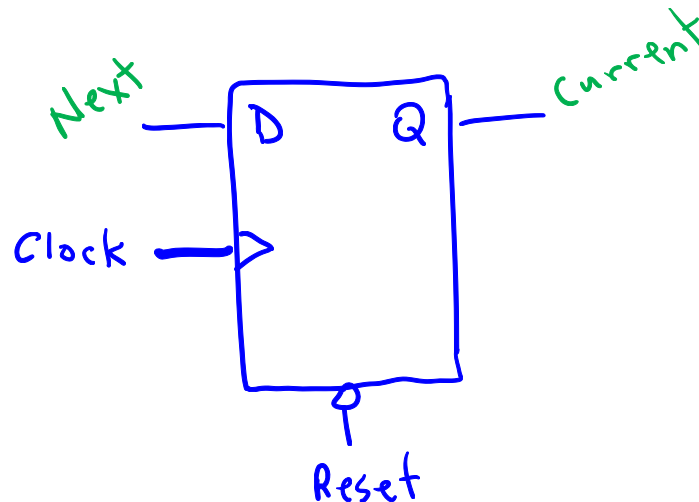




$x++;$
 $y = x \text{ mod } 10;$

y is between and

- 8 1 0 0 0
- 9 1 0 0 1
- A 10 1 0 1 0
- B 11 1 0 1 1
- C 12 1 1 0 0
- D 13 1 1 0 1

Odometer

ripple?

 

5 decimal digits are
modulo

$y = x \text{ mod } \underline{\hspace{2cm}}$

4-bit counter:

$2^4 =$


0 - F


0 - 9, A - F

Mod 10 Counter Example

- Decade counter
- Base 10 counter

Mod 10 Counter Example

 - ① Edge? 
- ② Synchron or asynch?
- ③ Priority?



■ Truth Table

		IN			OUT		Mode
clk	reset	ctrl	D	Q	Q		
0,1,falling	x	xx	x	Q			
rising	0	xx	x	0			
rising	1	00	x	Q			
rising	1	01	x	(Q+1) mod 10			
rising	1	10	D	D			
rising	1	11	x	0			



④ Why 2 resets?

Missing? —
—
—



Cascade Mod-10 counters?

2 Digit

Ripple Counter

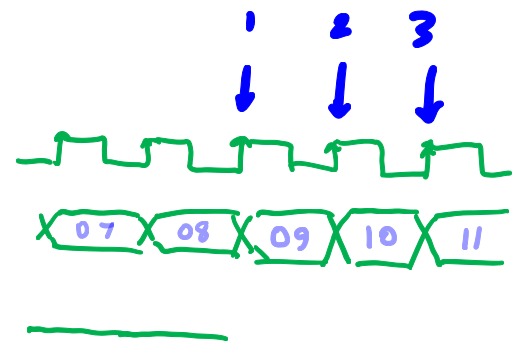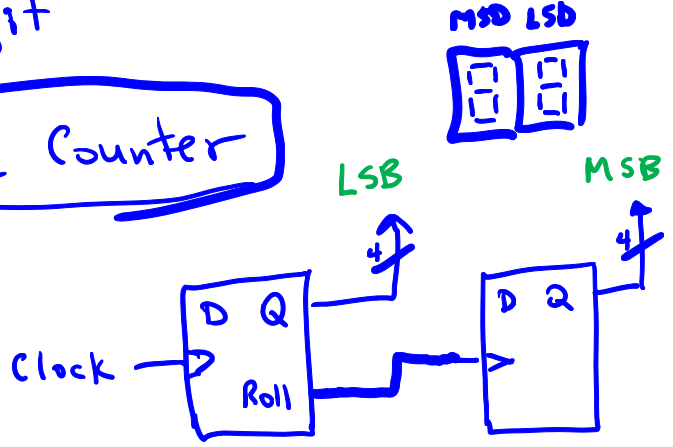

Sync Counter

 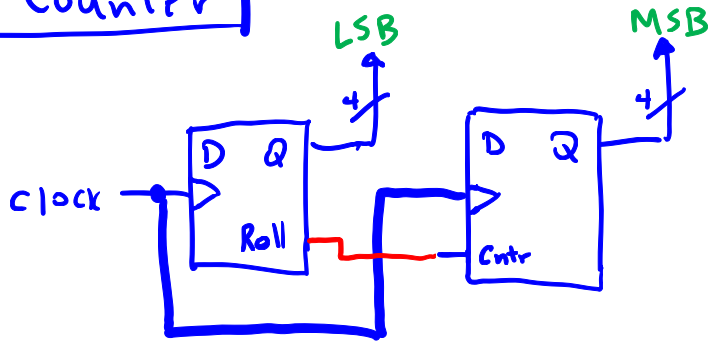



Handout:


Complete the Q trace in the following timing diagram based on the state table for the mod-10 counter.

↳ Do Handout

Timing Diagram




Mod 10 Counter - Timing Diagram

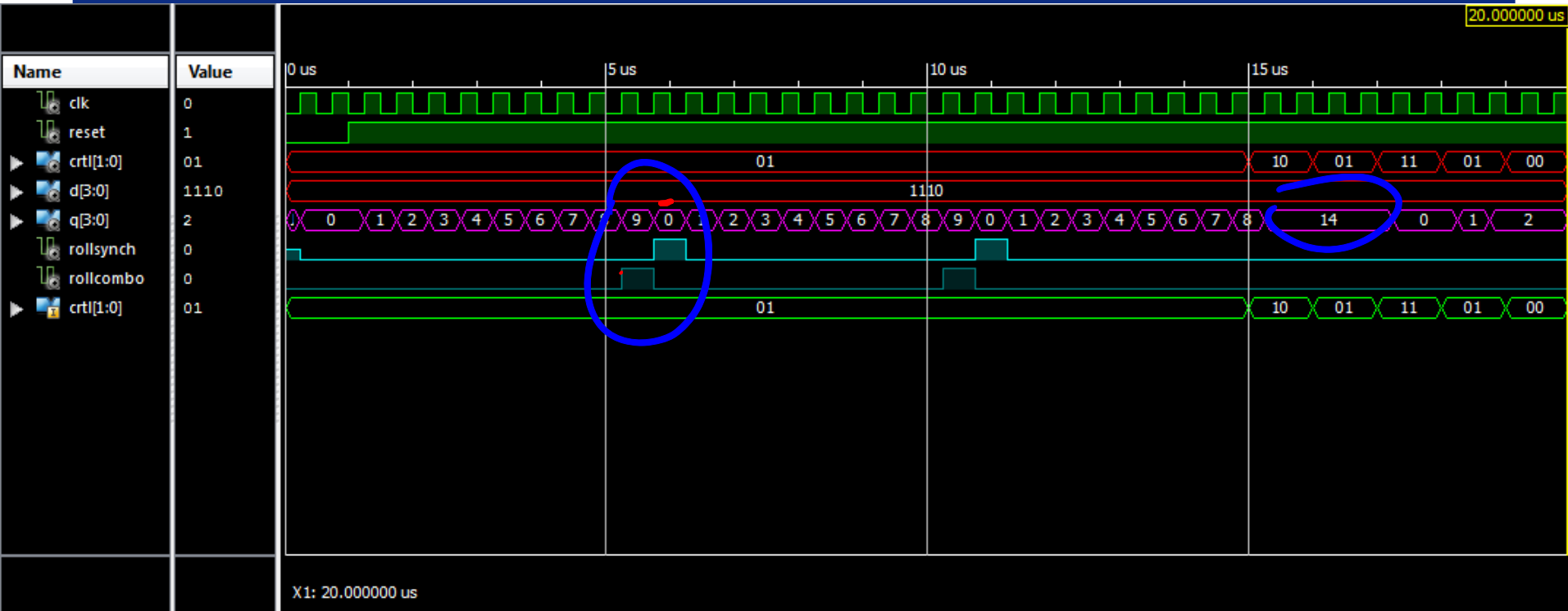




Mod 10 Counter - Timing Diagram

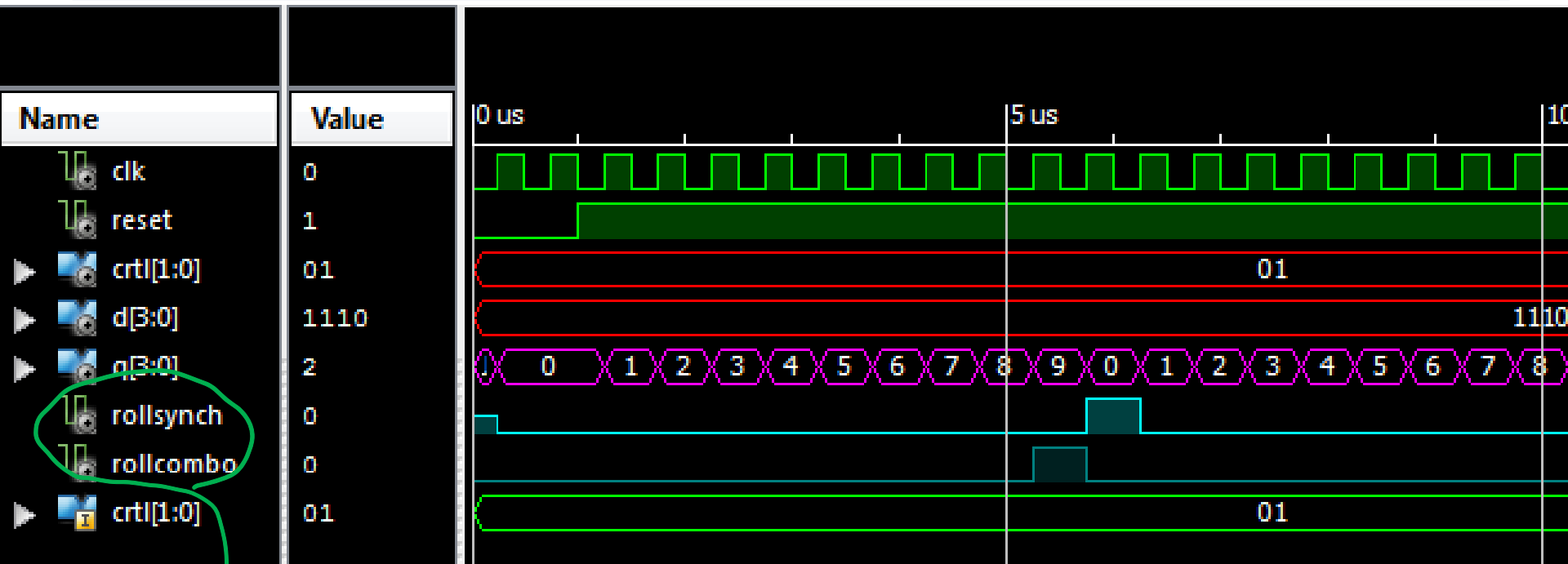

which is best for Ripple counter? **Roll** _____
 for Sync counter? **Roll** _____



Mod 10 Counter - Timing Diagram

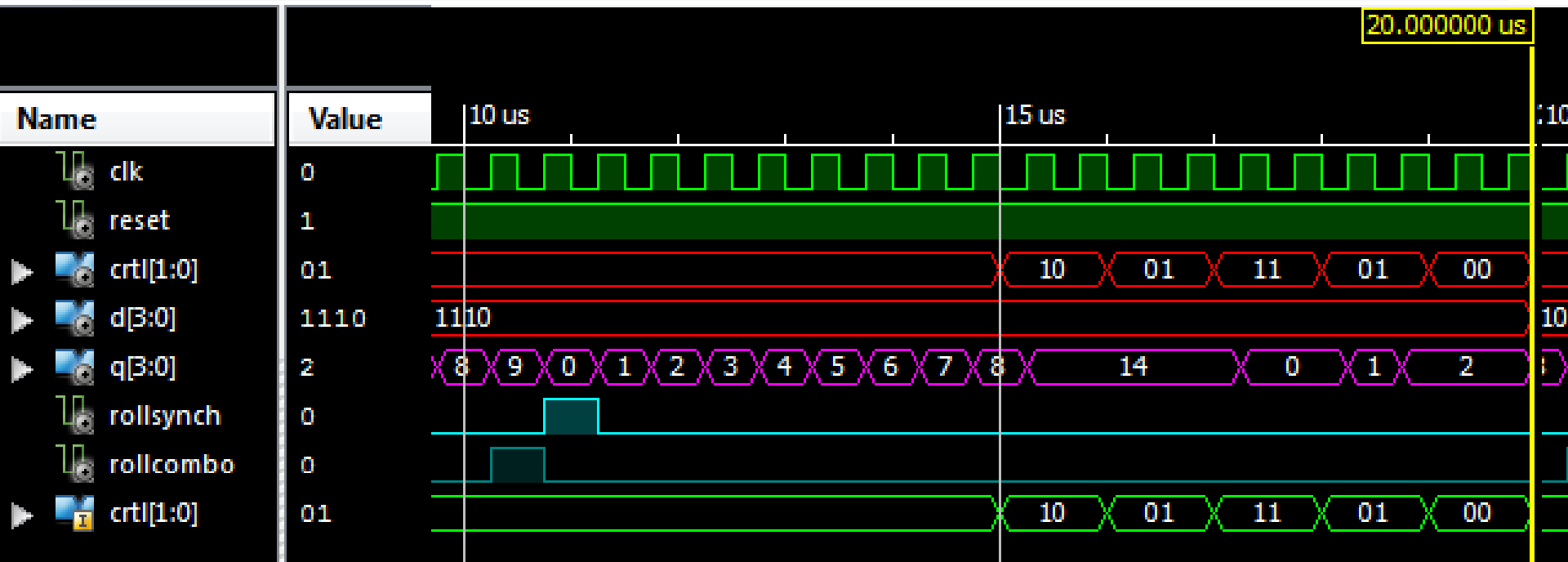




UNITED STATES
AIR FORCE
ACADEMY

Circuit Diagram




Circuit Diagram

- After completing the timing diagram, see if you can figure out how to construct the counter using the arrangement of devices show in the picture below.
 - You may assume that all these inputs are able to handle 4-bit values - to indicate this, draw a hash through the signal lines with a "4" next to it.
 - ~~■ You should not draw additional lines in this picture. Instead, label the wires with names and use these names to create logical connections between signals with the same name.~~
 - Draw a border around your circuit. The only signals that should cross the boundary are those which are part of the entity description.

 

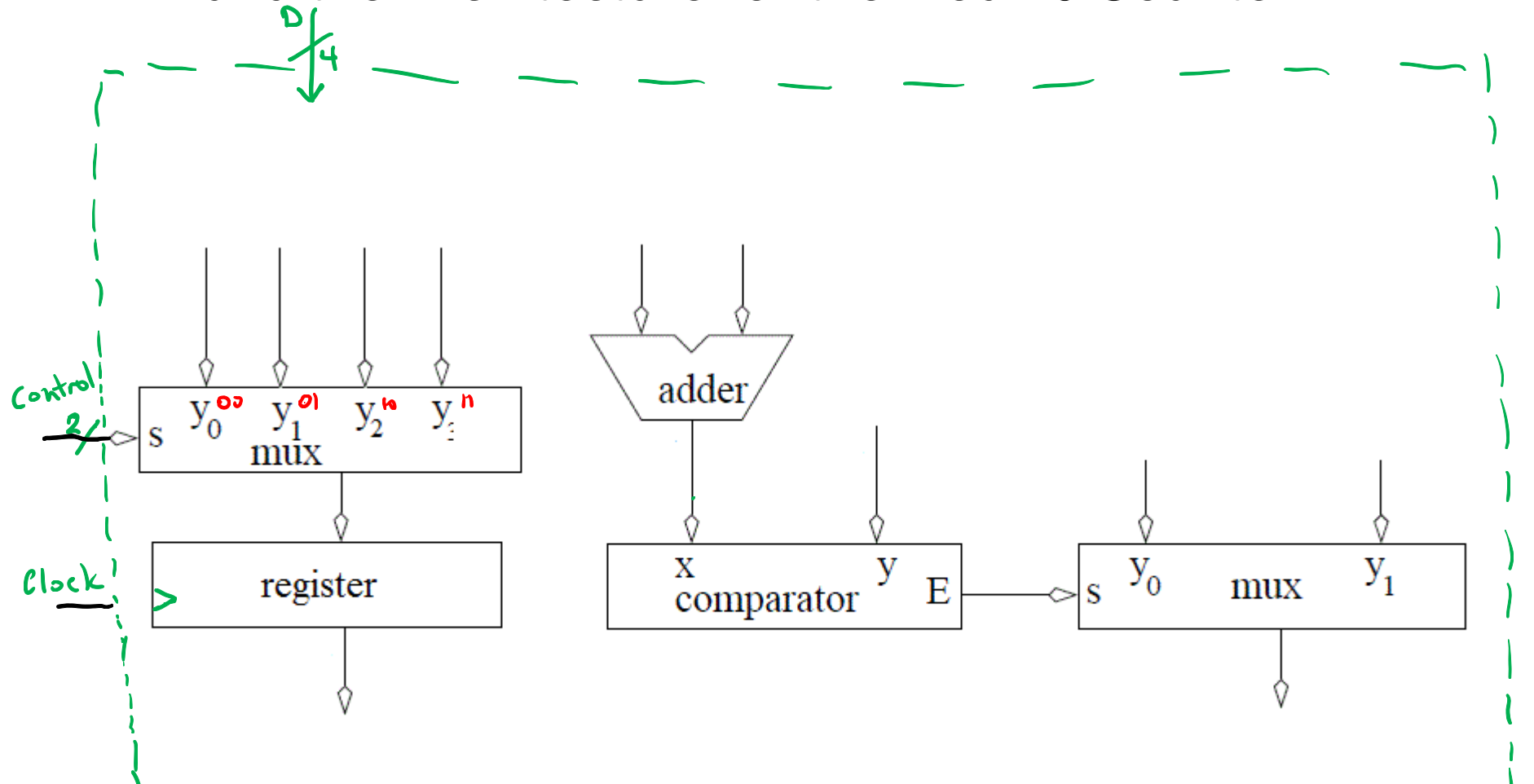■ Build the Architecture for the Mod 10 Counter





If Dr York says use
a mod-10 counter BBB to make a circuit
on a GK...

VHDL



Mod 10 Counter – VHDL Code Entity

entity lec4 is

```
Port(   clk: in  STD_LOGIC;  
       reset : in  STD_LOGIC;  
       ctrl: in  std_logic_vector(1 downto 0);  
       D: in  unsigned (3 downto 0);  
       Q: out unsigned (3 downto 0));
```

end lec4;

1. architecture behavior of lec4 is
2. signal rollSynch, rollCombo: STD_LOGIC;
3. signal processQ: unsigned (3 downto 0);
4. begin

Mod 10 Counter – VHDL Code Architecture

```
5. process(clk)
6.   begin
7.     if (rising_edge(clk)) then
8.       if (reset = '0') then
9.         processQ <= (others => '0');
10.        rollSynch <= '0';
11.      elsif ((processQ < 9) and (ctrl = "01")) then
12.        processQ <= processQ + 1;
13.        rollSynch <= '0';
14.      elsif ((processQ = 9) and (ctrl = "01")) then
15.        processQ <= (others => '0');
16.        rollSynch <= '1';
17.      elsif (ctrl = "10") then
18.        processQ <= D;
19.      elsif (ctrl = "11") then
20.        processQ <= (others => '0');
21.      end if;
22.    end if;
23.  end process;
24.  rollCombo <= '1' when (processQ = 9) else '0';
25.  Q <= processQ;
26. end behavior;
```


Always

Fix to bng

and

Roll Issue (Bug) with Roll Combo


"01" count up
"00" hold

 

If 2 cascaded
Synch Counters

Ideal Q₁Q₀
Actual Q₁Q₀

	07	08	09	09	10	11	12
Hold count							
Ideal Q ₁ Q ₀	07	08	09	<u>09</u>	<u>10</u>	<u>11</u>	<u>12</u>
Actual Q ₁ Q ₀	07	08	09	—	—	—	—

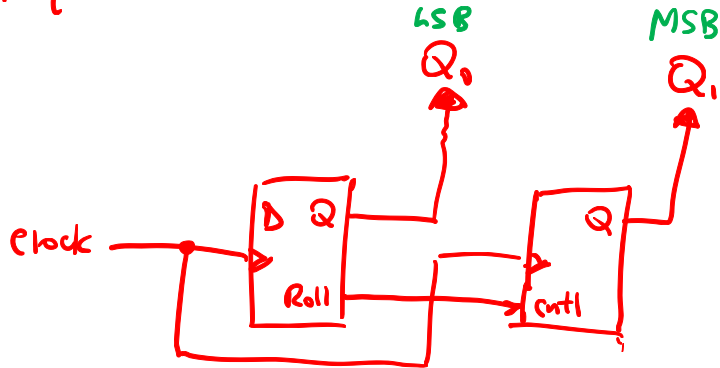



UNITED STATES
AIR FORCE
ACADEMY

General VHDL Rules

General VHDL Rules

- Introduce the following rules for designing in VHDL in order to write code that can be **synthesized**.
 - Never use processes for combinational logic.
 - ① ■ Only the clk should appear in the sensitivity list
 - ② ■ The outermost structure should be "if (rising_edge(clk)) then"
 - ③ ■ Inside this structure should be "if (reset = '0') then" to reinitialize the state element used by the process
 - The else clause of the reset element (the body) should consist of a set of **exclusive** signal conditions in an if/then case structure.
 - Any signal on the **left-hand** side of an assignment statement (in the body) may not be put on the **left-hand** side of any assignment statement outside the process.



UNITED STATES
AIR FORCE
ACADEMY

Adding Signals in Vivado

Adding Signals in Vivado

- Sometimes it is necessary to examine signals not directly visible in a design. In the Instances and Process subwindow, reveal the instances inside the lec4_tb by clicking on the arrow to the left lec4_tb.
 1. Reveal the signals inside the lec4 instance (called uut) by clicking on the label "uut".
 2. In the Objects subwindow select the signal that you want to observe on the timing diagram. In our case the ctrl signal.
 3. Drag and drop the signal into the timing diagram.
 4. In most cases you will have to restart the simulation to get a complete trace of the newly added signal.
 5. And the rerun it for the needed amount of time.



UNITED STATES
AIR FORCE
ACADEMY

Adding Signals in Vivado Simulator

The screenshot shows the Vivado Simulator interface with several key components annotated with red circles and numbers:

- 1**: Instance and Process Name list, highlighting the ' uut ' instance.
- 2**: Refresh button (circular arrow icon) next to the ' uut ' instance.
- 3**: Simulation Objects for uut table, highlighting the ' crt1[1:0] ' object with a value of ' 01 '.
- 4**: Object Name list, highlighting the ' crt1[1:0] ' object.
- 5**: Run button (play icon) in the simulation toolbar.
- 6**: Time scale dropdown menu set to ' 10.00us '.

The simulation waveform on the right shows signals: ' clk ' (green), ' reset ' (green), ' crt1[1:0] ' (red), ' d[3:0] ' (red), ' q[3:0] ' (purple), ' rollsynch ' (cyan), ' rollcombo ' (cyan), and ' crt1[1:0] ' (green). The time scale is 10.000000 us.

Console
ISim>
restart



go to HW4.pdf

- power switch
- USB cable
- Driver not installed